	Unit 5F Ohm's Law	Name:
gpb.org/physics-motion Main Ideas, Key Poin Questions: After watching the video segment, w down key points, main ideas, and bis questions. Summary: After w	vrite ig Notes:	Date: words and mathematically. terent materials may follow Ohm's Law or not. During the video segment, use words, phrases, or drawings to take notes. tere sentences explaining what you learned. there sentences explaining what you learned. there is to someone else, what would I say?"

Unit 5F\_Notes and Questions STUDENT Copyright © 2018 Georgia Public Broadcasting. All rights reserved. Use or distribution by an unintended recipient is prohibited.



## Unit 5F Ohm's Law *Questions to Consider*

Date:


Name:

 Answer the following.

 1. What is voltage, what is current, and what is resistance?

2. Name two ways that knowing Ohm's Law could be helpful for someone designing an electrical circuit.

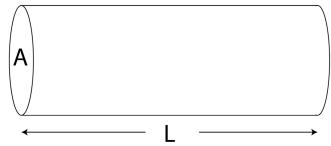3. When current flows through a wire of length L and cross-sectional area A, the resistance in the wire (choose one):



- a. Is proportional to L and A
- **b.** Is inversely proportional to L and A
- c. Is proportional to L and inversely proportional to A
- d. Is inversely proportional to L and proportional to A
- 4. Using a material that is 'Ohmic' (it follows Ohm's Law), you make a circuit using wire, a battery, and a resistor. After measuring V, I, and R across the circuit, you switch out the original resistor with one 3 times more resistive. When you measure V, I, and R again, how will the new values compare to the old?





Unit 5F Ohm's Law *Questions to Consider* 

Date:

## Answer the following.

5. You are given two materials, A and B, and told that one follows Ohm's Law and one does not. Describe an experiment you could run to figure out which is which.

6. Write out three different (but equivalent) ways of expressing Ohm's Law mathematically.

- 7. If doubling the voltage across an Ohmic resistor doubles the current in the resistor, then
  - a. The resistor value decreased
  - b. The resistor value increased
  - c. The resistor value stayed the same
  - d. The change in resistor value can't be determined