Name _____


- Electric Current is
- Current flows when
- To create this difference,

Charge Pumps (sources of _____): 1. photocell examples:

- 2. battery -
- 3. generator examples:

Electric Circuit:

- •
- •

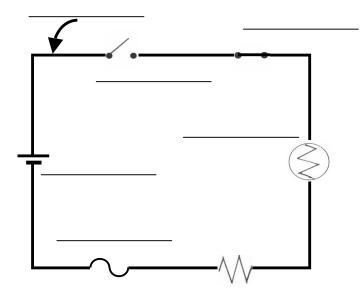

A _____ is a device using electrical energy. In a load, work is done _____ the electrons, and the PE of the electrons (increases, decreases).

Since it opposes the flow of current, a load is a type of



Electric energy (from charge pumps) can be converted into: (from demos)

circuit diagram:

Fact or Fiction? When you turn on a light switch, electrons move rapidly from the socket to the lamp to light the bulb.

_____ is always a side effect of _____ (because of electron _____).

- A potential difference
- An electric field

Direct Current (dc)

•

Alternating Current (ac)

- •
- •

Conventional Current -

Show What You Know -